

C9 Unravel the general characteristics of chaotic systems by exploring chaotic circuits

SUPPLEMENTARY INFORMATION

Experimenter: Zweig, Wong 20980066

Participant: Runbing Mo 20980131

Date: 2022.05.11

Contents

| | | |
|----------|---|----------|
| 1 | Materials and instruments | 2 |
| 2 | Exp.1 Chua's circuit | 2 |
| 2.1 | Main parameters | 2 |
| 2.1.1 | Numerical calculation | 2 |
| 2.1.2 | Simulation | 2 |
| 2.1.3 | Experiment | 2 |
| 3 | Exp.2 Lorentz's circuit | 4 |
| 3.1 | Main parameters | 4 |
| 3.1.1 | Numerical calculation | 4 |
| 3.1.2 | Simulation | 4 |
| 4 | Reflection question | 5 |
| 4.1 | Application of chaotic circuits | 5 |
| 5 | Data and code availability | 5 |

1 Materials and instruments

Table S1: **Materials and instruments**

| Name | Total | Model and parameters |
|-----------------------------|-------|---------------------------|
| <i>Anaconda</i> | 1 | <i>version</i> 4.10.3 |
| <i>Multisim</i> | 1 | <i>version</i> 16.0 |
| <i>LTspice</i> | 1 | <i>version</i> 17.0.34 |
| Breadboard | 1 | |
| Various Electric components | | (Details in next section) |

2 Exp.1 Chua's circuit

2.1 Main parameters

2.1.1 Numerical calculation

Parameters of different patterns adopted in the numerical calculation are summarized in Tab. [S2](#). These parameters can also be explored in the Jupyter Notebook provided in the thesis.

Table S2: **Parameters of different patterns, numerical calculation**

| pattern | m_1 | m_2 | α | β |
|----------------------|-------|-------|----------|---------|
| line | -2.0 | -1.3 | 26 | 12 |
| limit ring | -0.5 | 1.0 | 13 | 13 |
| double attractors | -1.1 | -0.7 | 21 | 36 |
| 1st single attractor | -1.1 | -0.7 | 21 | 31 |
| 2nd single attractor | -1.1 | -0.7 | 21 | 15 |

2.1.2 Simulation

To generate different chaotic patterns, we adjusted the resistance value of R_7 . The different resistance values of the corresponding patterns for the two circuits are summarized in Tab. [S3](#) and Tab. [S4](#), respectively.

2.1.3 Experiment

We built the two circuits and adjusted the resistance value of R_7 to get different chaotic patterns. Parameters of electric components are summarized in Tab. [S5](#) Different resistance value of corresponding patterns for the two circuits are summarized in Tab. [S6](#) and Tab. [S7](#), respectively.

Table S3: **Parameters of different patterns, simulation of circuit I**

| <i>pattern</i> | R_7 |
|----------------------|--------------------------|
| line | $0.00\% \times 2k\Omega$ |
| limit ring | $76.8\% \times 2k\Omega$ |
| double attractors | $86.8\% \times 2k\Omega$ |
| 1st single attractor | $94.8\% \times 2k\Omega$ |
| 2nd single attractor | $96.0\% \times 2k\Omega$ |

Table S4: **Parameters of different patterns, simulation of circuit II**

| <i>pattern</i> | R_7 |
|----------------------|--------------------------|
| line | $0.00\% \times 2k\Omega$ |
| limit ring | $52.0\% \times 2k\Omega$ |
| double attractors | $78.0\% \times 2k\Omega$ |
| 1st single attractor | $80.6\% \times 2k\Omega$ |
| 2nd single attractor | Missing |

Table S5: **Parameters of electric components**

| Name | Total | Value |
|-------|-------|--------------------|
| L_1 | 1 | $21.005mH$ |
| C_1 | 1 | $10.277nF$ |
| C_2 | 1 | $91.104nF$ |
| R_1 | 1 | 218.43Ω |
| R_2 | 1 | 220.13Ω |
| R_3 | 1 | $22.060k\Omega$ |
| R_4 | 1 | $21.923k\Omega$ |
| R_5 | 1 | $2.2012k\Omega$ |
| R_6 | 1 | $3.2625k\Omega$ |
| R_7 | 1 | $Max1.9650k\Omega$ |

Table S6: **Parameters of different patterns, experiment of circuit I**

| <i>pattern</i> | R_7 |
|----------------------|-----------------|
| line | 0.00Ω |
| limit ring | 1498.20Ω |
| double attractors | 1880.32Ω |
| 1st single attractor | 1907.20Ω |
| 2nd single attractor | Misssing |

Table S7: Parameters of different patterns, experiment of circuit II

| <i>pattern</i> | R_7 |
|----------------------|------------------|
| line | 0.00 Ω |
| limit ring | 1408.01 Ω |
| double attractors | 1563.20 Ω |
| 1st single attractor | 1661.41 Ω |
| 2nd single attractor | 1802.03 Ω |

3 Exp.2 Lorentz's circuit

3.1 Main parameters

3.1.1 Numerical calculation

Parameters for generating the Lorentz butterfly in the numerical calculation are summarized in Tab. S8. These parameters can also be explored in the Jupyter Notebook provided in the thesis.

Table S8: Parameters of Lorentz butterfly, numerical calculation

| <i>pattern</i> | α | β | γ |
|----------------|----------|---------|----------|
| butterfly | 10.0 | 28.0 | 2.8 |

3.1.2 Simulation

The simulation circuit (Fig. S1a) and the corresponding parameters (Fig. S1b) to generate the Lorentz butterfly in LTspice are shown below. This schematic referenced Jim's work, who kindly provided his schematic on his website(www.chaotic-circuits.com). We especially thanks to him.

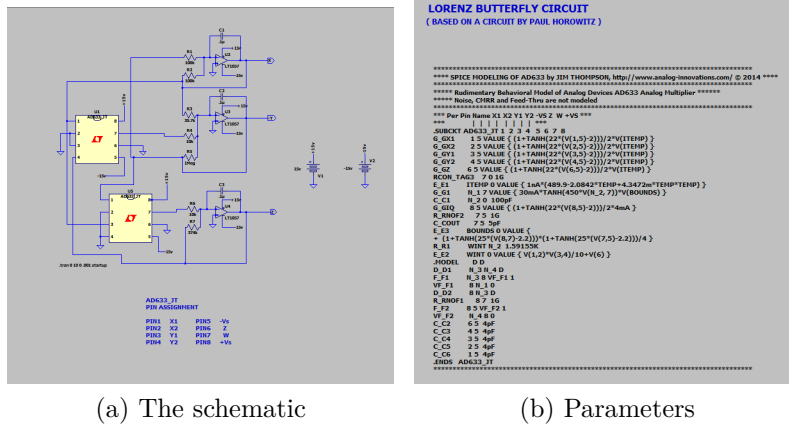


Figure S1: Simulation of the Lorentz circuit

4 Reflection question

4.1 Application of chaotic circuits

1. As mentioned in the thesis, when investigating other much more complex chaotic systems, it is a pretty effective way to create and operate on an electronic "analog" instead of directly working with the actual system, which may be difficult or impossible to control.
2. Chaotic systems can be used for socalled chaos encryption, which means hiding data signals within a chaotic signal to ensure the security[1].
3. They can also be used for true random bit generation taking advantages of their long-term unpredictability[2].
4. In robotics, chaotic signals are being used in neural control networks or as chaotic path generators [3].

5 Data and code availability

Data and code are available at <https://github.com/Zweig-Wong/SYSU-PHY-EXP>

Reference

1. C. Tanougast, in *Chaos-Based Cryptography*, ed. by L. Kocarev, S. Lian, red. by J. Kacprzyk (Springer Berlin Heidelberg, Berlin, Heidelberg, 2011), vol. 354, pp. 297–330, ISBN: 978-3-642-20541-5 978-3-642-20542-2, (2022; http://link.springer.com/10.1007/978-3-642-20542-2_9) (cit. on p. 5).
2. R. M. Nguimdo *et al.*, *Optics Express* **20**, 28603, ISSN: 1094-4087, (2022; <https://opg.optica.org/oe/abstract.cfm?uri=oe-20-27-28603>) (Dec. 17, 2012) (cit. on p. 5).
3. S. Steingrube, M. Timme, F. Wörgötter, P. Manoonpong, *Nature Physics* **6**, 224–230, ISSN: 1745-2473, 1745-2481, (2022; <http://www.nature.com/articles/nphys1508>) (Mar. 2010) (cit. on p. 5).